
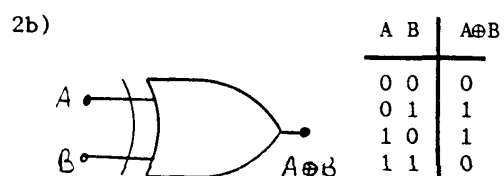


**Problem Set Solutions**


1. Make a conversion table from Decimal (Base 10) to Binary (Base 2) from zero to thirty-five. Zero fill the binary numbers to generate six bits.

NON-ZERO FILLED		ZERO FILLED	
Decimal	Binary	Decimal	Binary
00	0	00	0 0 0 0 0 0
01	1	01	0 0 0 0 0 1
02	1 0	02	0 0 0 0 1 0
03	1 1	03	0 0 0 0 1 1
04	1 0 0	04	0 0 0 1 0 0
05	1 0 1	05	0 0 0 1 0 1
06	1 1 0	06	0 0 0 1 1 0
07	1 1 1	07	0 0 0 1 1 1
08	1 0 0 0	08	0 0 1 0 0 0
09	1 0 0 1	09	0 0 1 0 0 1
10	1 0 1 0	10	0 0 1 0 1 0
11	1 0 1 1	11	0 0 1 0 1 1
12	1 1 0 0	12	0 0 1 1 0 0
13	1 1 0 1	13	0 0 1 1 0 1
14	1 1 1 0	14	0 0 1 1 1 0
15	1 1 1 1	15	0 0 1 1 1 1
16	1 0 0 0 0	16	0 1 0 0 0 0
17	1 0 0 0 1	17	0 1 0 0 0 1
18	1 0 0 1 0	18	0 1 0 0 1 0
19	1 0 0 1 1	19	0 1 0 0 1 1
20	1 0 1 0 0	20	0 1 0 1 0 0
21	1 0 1 0 1	21	0 1 0 1 0 1
22	1 0 1 1 0	22	0 1 0 1 1 0
23	1 0 1 1 1	23	0 1 0 1 1 1
24	1 1 0 0 0	24	0 1 1 0 0 0
25	1 1 0 0 1	25	0 1 1 0 0 1
26	1 1 0 1 0	26	0 1 1 0 1 0
27	1 1 0 1 1	27	0 1 1 0 1 1
28	1 1 1 0 0	28	0 1 1 1 0 0
29	1 1 1 0 1	29	0 1 1 1 0 1
30	1 1 1 1 0	30	0 1 1 1 1 0
31	1 1 1 1 1	31	0 1 1 1 1 1
32	1 0 0 0 0 0	32	1 0 0 0 0 0
33	1 0 0 0 0 1	33	1 0 0 0 0 1
34	1 0 0 0 1 0	34	1 0 0 0 1 0
35	1 0 0 0 1 1	35	1 0 0 0 1 1

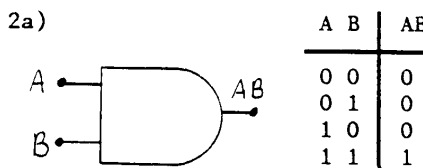2. Draw the following gates and construct the truth tables for these gates.




2c)

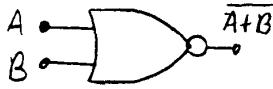


A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

2d)

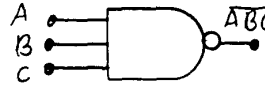


A	B	C	$\overline{ABC}$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

2e)

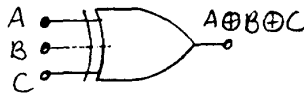

A	B	C	$A\oplus B\oplus C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

2f)

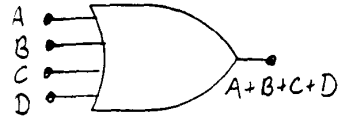


A	B	C	D	$A+B+C+D$
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

3. Draw the gates which represent the following Boolean symbols.


3a)




3b)

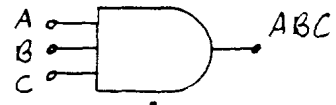


3c)

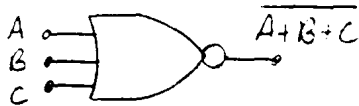

3d)

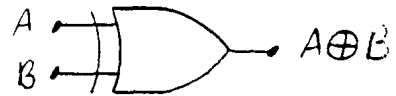

3e)

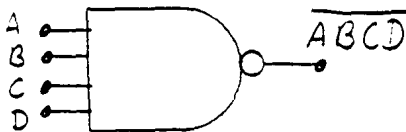

4. Prove the following Boolean Identities using Truth Tables.

4a)  $0A = 0$

A	0	0A
0	0	0
1	0	0

↑ Answer

4c)  $AA = A$

A	A	AA
0	0	0
1	1	1

↑ Verifies

4e)  $(A+B)+C = A+(B+C)$

A	B	C	A+B	(A+B)+C	B+C	A+(B+C)
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	1	0	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

↑ Verifies

4f)  $A(\bar{A}+B) = AB$

A	B	$\bar{A}$	$\bar{A}+B$	$A(\bar{A}+B)$	AB
0	0	1	1	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	1	0	1	1	1

↑ Verifies

4g)  $A+BC = (A+B)(A+C)$

A	B	C	BC	A+BC	A+B	A+C	$(A+B)(A+C)$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	0	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

↑ Verifies

5. Prove the following equivalencies using Boolean algebra.

5a)  $(A+B)(A+C)$

$$\begin{aligned}
 &= AA + AC + AB + BC && \text{Expand out (Distrib OR)} \\
 &= A + AC + AB + BC && \text{Idempotent AND Law} \\
 &= 1A + AC + AB + BC && \text{Identity AND Law} \\
 &= A(1+C) + AB + BC && \text{Distributive OR Law} \\
 &= A(1) + AB + BC && \text{Null OR Law} \\
 &= A(1+B) + BC && \text{Distributive OR Law} \\
 &= A(1) + BC && \text{Null OR Law} \\
 &= A + BC && \text{Identity AND Law} \\
 \text{Therefore } &A+BC = (A+B)(A+C)
 \end{aligned}$$

$$\begin{aligned}
 5b) \quad & A(\bar{A} + B) \\
 & = A\bar{A} + AB && \text{Distributive OR Law} \\
 & = 0 + AB && \text{Inverse AND Law} \\
 & = AB && \text{Identity OR Law} \\
 \text{Therefore} \quad & A(\bar{A} + B) = AB
 \end{aligned}$$

$$\begin{aligned}
 5c) \quad & (A + \overline{B+C})\bar{A} \\
 & = A\bar{A} + \overline{B+C}\bar{A} && \text{Distributive OR Law} \\
 & = 0 + \overline{B+C}\bar{A} && \text{Inverse AND Law} \\
 & = \bar{A}\overline{B+C} && \text{Commutative AND Law} \\
 & = \bar{A}\bar{B}\bar{C} && \text{De Morgan's OR Law} \\
 & = \overline{A+B+C} && \text{De Morgan's OR Law}
 \end{aligned}$$

$$\begin{aligned}
 5d) \quad & AB + C + \overline{AB}CD + CC \\
 & = AB + C + \overline{AB}CD + C && \text{Idempotent AND Law} \\
 & = AB + \overline{AB}CD + C && \text{Idempotent OR Law} \\
 & = K + \overline{K}CD + C && \text{Substitution } K=AB \\
 & = K + CD + C && \text{Inclusion OR Law} \\
 & = AB + CD + C && \text{Substitution } AB=K \\
 & = AB + C && \text{Absorption OR Law}
 \end{aligned}$$

$$\begin{aligned}
 5e) \quad & \overline{A\bar{B}(B+C)} \\
 & = \bar{A} + \overline{\overline{B(B+C)}} && \text{DeMorgan's AND Law} \\
 & = \bar{A} + B(B+C) && \text{Double Inversion} \\
 & = \bar{A} + B && \text{Absorption AND Law}
 \end{aligned}$$

$$\begin{aligned}
 5f) \quad & A\bar{B} + A\bar{C} + BC \\
 & = A(\bar{B} + \bar{C}) + BC && \text{Distributive OR Law} \\
 & = A\overline{BC} + BC && \text{DeMorgan's AND Law} \\
 & = A + BC && \text{Inclusion OR Law}
 \end{aligned}$$


$$\begin{aligned}
 5g) \quad & \overline{\overline{A\bar{B}\bar{A}\bar{C}}} \\
 & = \overline{\overline{\bar{A}\bar{B}\bar{C}}} && \text{Idempotent AND Law} \\
 & = \overline{A+B+C} && \text{DeMorgan's OR Law} \\
 & = A+B+C && \text{Double Inversion}
 \end{aligned}$$

$$\begin{aligned}
 5h) \quad & \overline{(\bar{A} + \bar{B} + \bar{C})C} \\
 & = \overline{\overline{A\bar{B}\bar{C} + C}} && \text{De Morgan's AND Law} \\
 & = A\bar{B}\bar{C} + \bar{C} && \text{Double Inversion} \\
 & = A\bar{B} + \bar{C} && \text{Inclusion OR Law}
 \end{aligned}$$


6. Write both sum of products and product of sums Boolean expressions for output Z using the truth table shown. Draw a logic diagram for both circuits.

Sop:  $\bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$

B	C	Z
0	0	0
0	1	0
1	0	1
1	1	0
0	0	1
0	1	1
1	0	0
1	1	0

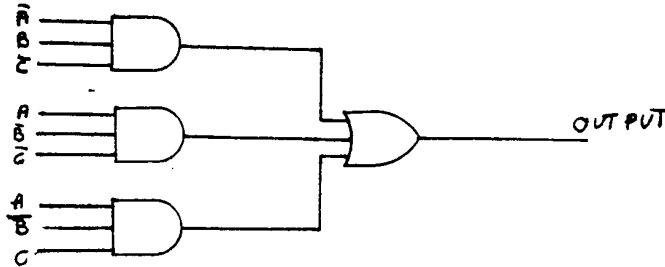


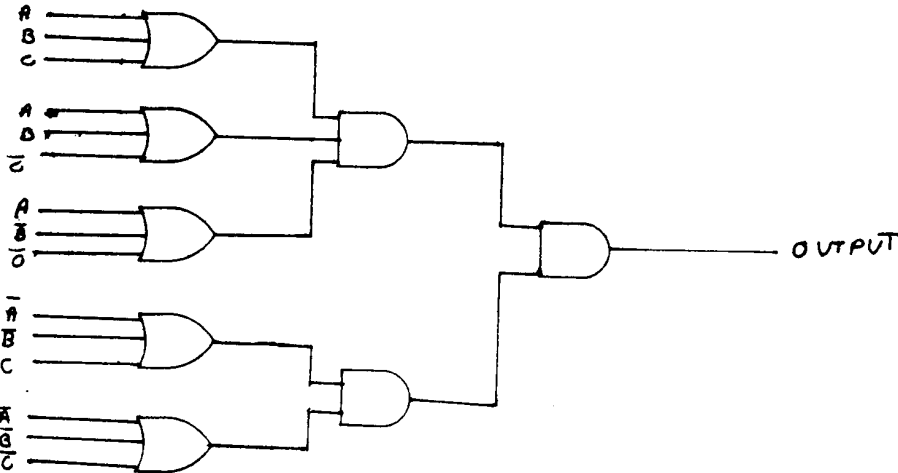POS =  $(A+B+C)(A+B+\bar{C})(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$




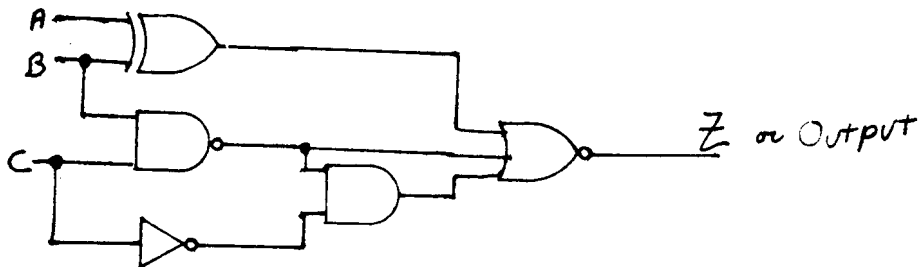7. Draw a logic diagram for the following Boolean Expression.

$Z = \overline{A \oplus B + \bar{B}C + \bar{B}C\bar{C}}$



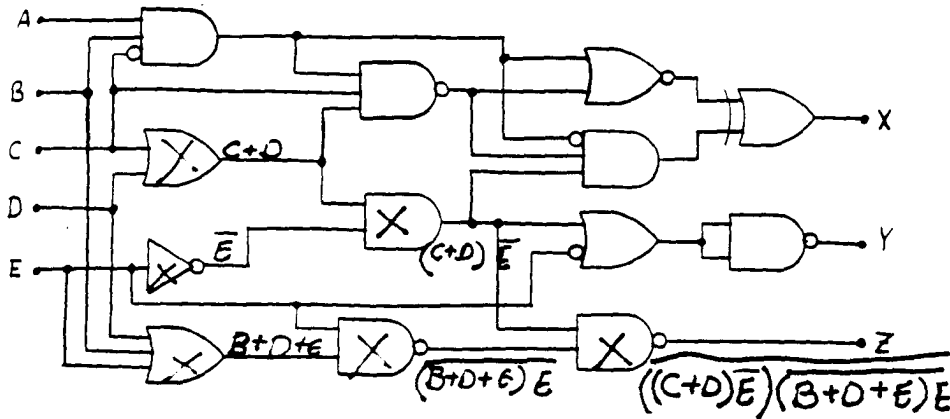8. Write a Boolean Expression for Output Z.



$$Z = \overline{((C+D)\bar{E})(B+D+E)\bar{E}}$$

9. Construct the truth table for the 3 to 8 decoder of Figure 2.13a.

A	B	C	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

10. Construct a 4-bit adder using logic gates.

